

Hall Ticket Number:

--	--	--	--	--	--	--	--	--

II/IV B.Tech (Supplementary) DEGREE EXAMINATION

April, 2017

Fourth Semester

Time: Three Hours

Common for CSE & IT
Electronic Devices & Circuits

Maximum : 60 Marks

Answer Question No.1 compulsorily.

(1X12 = 12 Marks)

Answer ONE question from each unit.

(4X12=48 Marks)

1. Answer all questions

(1X12=12 Marks)

- What do you mean by cut in voltage in a diode?
- What are the applications of UJT?
- What is Zener mechanism?
- Draw the pin diagram of 741 IC.
- Define PIV. What is PIV of a halfwave rectifier?
- For a JFET, $I_{DSS} = 15\text{mA}$, $V_p = -5\text{V}$, determine I_D for $V_{GS} = -3\text{V}$.
- What are the characteristics of JFET?
- What are the characteristics of a trans-conductance amplifier?
- Give the expression for frequency of operation for (i) RC Phase shift oscillator (ii) Hartley Oscillator.
- What are the ideal characteristics of an op-amp?
- Define Slew rate.
- Draw the circuit of differentiator using op-amp and write the expression for output voltage.

UNIT I

- Explain the working principle of a centre tapped full wave rectifier with neat waveforms. 6M
 - Derive the expressions for input resistance, output resistance, voltage gain and current gain of a CE transistor amplifier using h-parameters. 6M
- (OR)
- Derive the stability factor S for an (i) Emitter stabilized bias circuit (ii) Fixed Bias circuit for a BJT. 8M
 - What is Early effect? What are its consequences? 4M

UNIT II

- Explain the operation of Enhancement type MOSFET. 6M
 - A self-biased p-channel JFET has a pinch off voltage $V_p = 5\text{V}$, $I_{DSS} = -12\text{mA}$, $V_{DD} = -12\text{V}$. Determine the values of R_D and R_S so that the drain current $I_D = -5\text{mA}$ and $V_{DS} = 6\text{V}$. 6M
- (OR)
- Explain the operation of UJT and also plot emitter characteristics indicating various regions. 6M
 - Explain the operation of n-channel JFET indicating its regions of operation. 6M

UNIT III

- Explain the concept of feedback. Derive an expression for transfer gain with feedback. 8M
 - What are the general characteristics of negative feedback amplifier? 4M
- (OR)
- State and explain Barkhausen criteria. 4M
 - Derive the expression for the frequency of oscillations of a Wien Bridge oscillator. 8M

UNIT IV

- Derive an expression for Common Mode Rejection Ratio for a differential amplifier using BJT. 6M
 - Explain the operation of the following circuits built using op-amp (i) Summing Amplifier (ii) Subtractor. 6M
- (OR)
- Explain the operation of Voltage Controlled Oscillator with a neat block diagram. 6M
 - Design a differentiator circuit that will differentiate an input signal with $f_{\max} = 200\text{Hz}$. Also, draw the output waveform for a sine wave of 1V at 200Hz applied to the differentiator. 6M